




Computer Systems

Lecture 02: Logic Gates



THE UNIVERSITY
of ADELAIDE


Our Journey

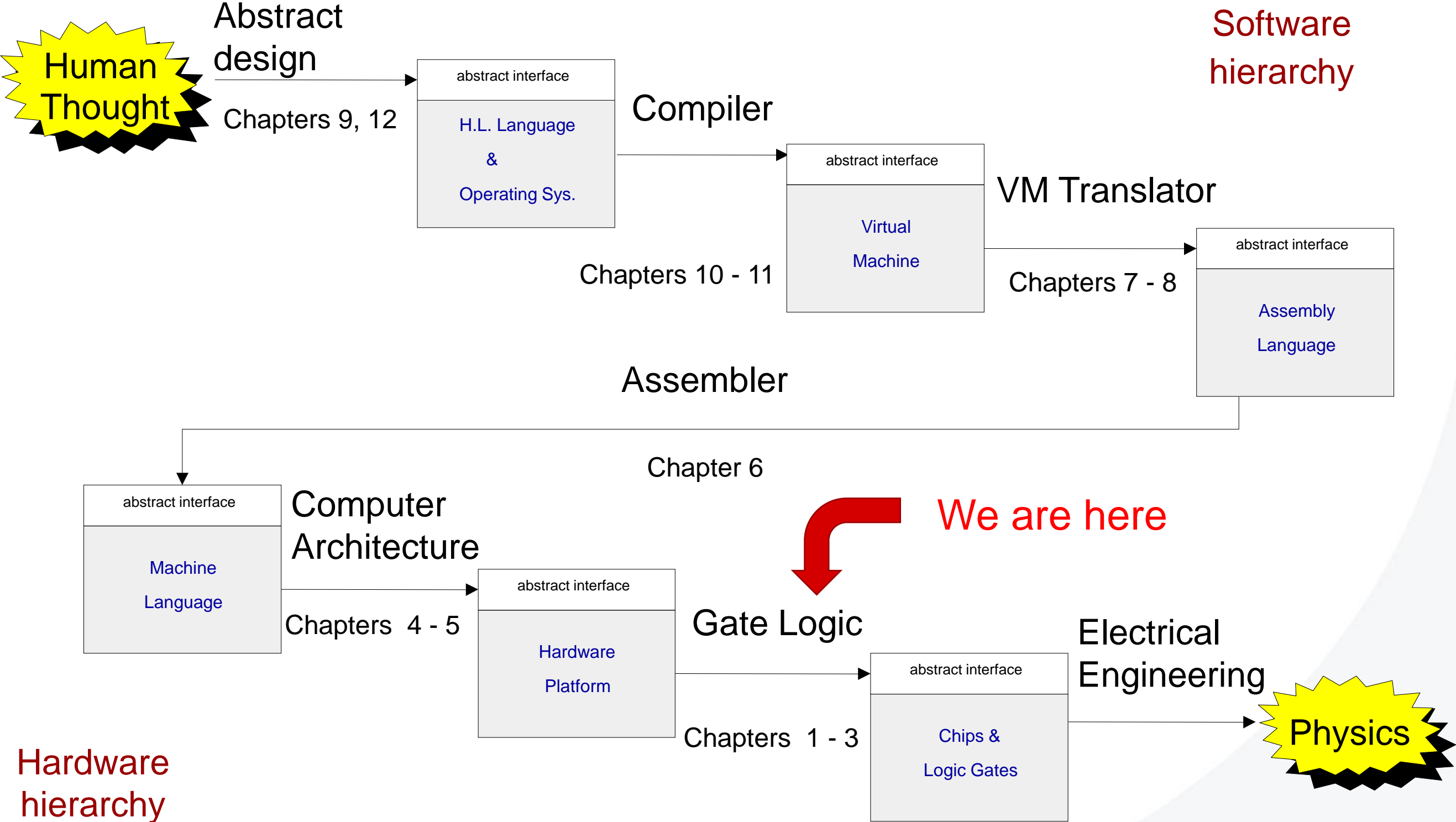

(Abstraction–implementation paradigm)

Review: Gate Logic


Interface

 


| a | b | out |
|---|---|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

(Truth table)

Implementation

 

In Workshops You Will Do:

 

```
CHIP Xor {  
  IN a, b;  
  OUT out;
```

PARTS:

```
Not(in=a, out=na);  
Not(in=b, out=nb);  
And(a=na, b=b, out=c);  
And(a=a, b=nb, out=d);  
Or(a=c, b=d, out=out);
```

```
}
```



All Boolean functions of 2 variables

| Function | x | 0 | 0 | 1 | 1 |
|--|-------------------------------------|---|---|---|---|
| | y | 0 | 1 | 0 | 1 |
| Constant 0 $\leftrightarrow x \cdot \bar{x}$ | 0 | 0 | 0 | 0 | 0 |
| x And y | $x \cdot y$ | 0 | 0 | 0 | 1 |
| x And Not y | $x \cdot \bar{y}$ | 0 | 0 | 1 | 0 |
| x | x | 0 | 0 | 1 | 1 |
| Not x And y | $\bar{x} \cdot y$ | 0 | 1 | 0 | 0 |
| y | y | 0 | 1 | 0 | 1 |
| x Xor y (Add / Difference) | $x \cdot \bar{y} + \bar{x} \cdot y$ | 0 | 1 | 1 | 0 |
| x Or y | $x + y$ | 0 | 1 | 1 | 1 |
| x Nor y | $\overline{x + y}$ | 1 | 0 | 0 | 0 |
| x Xnor y (Equivalence) | $x \cdot y + \bar{x} \cdot \bar{y}$ | 1 | 0 | 0 | 1 |
| Not y | \bar{y} | 1 | 0 | 1 | 0 |
| x Or Not y (If y then x) | $x + \bar{y}$ | 1 | 0 | 1 | 1 |
| Not x | \bar{x} | 1 | 1 | 0 | 0 |
| Not x Or y (If y then x) | $\bar{x} + y$ | 1 | 1 | 0 | 1 |
| x Nand y | $\overline{x \cdot y}$ | 1 | 1 | 1 | 0 |
| Constant 1 $\leftrightarrow x + \bar{x}$ | 1 | 1 | 1 | 1 | 1 |

Canonical Form: representation of a Boolean function in terms of And, Or, and Not

We can construct a canonical representation of any Boolean function with:

- And (symbol “dot product” Example: $x \cdot y$)
- Or (symbol “plus sign” Example: $x + y$)
- Not (symbol “bar on top” Example: \bar{x})

How?


- Sum of Product (SoP) ← focus in this course
- Product of Sum (PoS)
- Karnaugh Map (K-map)

...



Canonical Form – Sum of Product (SoP)

| a | b | sel | out |
|---|---|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

 

Exercise at the end!


$$\text{out} = (\bar{a}.b.sel) + (a.\bar{b}.\bar{sel}) + (a.b.\bar{sel}) + (a.b.sel)$$

1. Find all lines with out = 1, ignore all lines with out = 0.
2. Write inputs in product (And), if the input is 1 write as it is, otherwise, write in bar (Not) form.
3. Repeat 2. for each line with out = 1.
4. Use sum (Or) to connect each term.



Canonical Form – Product of Sum (PoS)

| a | b | sel | out |
|---|---|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

 


$$\text{out} = (a + b + \text{sel}).(a + b + \overline{\text{sel}}). \\ (a + \bar{b} + \text{sel}).(\bar{a} + b + \overline{\text{sel}})$$

1. Find all lines with out = 0, ignore all lines with out = 1.
2. Write inputs in sum (Or), if the input is 0 write as it is, otherwise, write in bar (Not).
3. Repeat 2. for each line with out = 0.
4. Use product (And) to connect each term.



Canonical Form – Karnaugh Map (K-map)

| a | b | sel | out |
|---|---|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

 

| a/b sel | | 00 | 01 | 11 | 10 |
|------------|---|----|----|----|----|
| 0 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 |

$$\text{out} = (\overline{a} \cdot \overline{\text{sel}}) + (b \cdot \text{sel})$$

K-map is one of the systematic way to simplify the Boolean expression.

In this course, we will not ask for simplification of Boolean expressions.

For curiosity please read: <https://www.allaboutcircuits.com/textbook/digital/chpt-8/logic-simplification-karnaugh-maps/>




How to construct And, Or and Not from Nand



From this



| A | B | out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

 




$$out = \overline{A \cdot B}$$

Formal proof in Textbook Appendix A1.3

How to construct And, Or and Not from Nand




From this

   

| A | B | out |
|--------------|--------------|--------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

 Have A and B
commonly
connected, A and
B always the
same



$$out = \overline{A \cdot B}$$

Formal proof in Textbook Appendix A1.3


How to construct And, Or and Not from Nand



From this



| A | B | out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

 

$$out = \overline{A \cdot B}$$

Formal proof in Textbook Appendix A1.3


How to construct And, Or and Not from Nand




From this

| A | B | out | $\overline{\text{out}}$ |
|---|---|-----|-------------------------|
| 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |


Add one Not gate to the out

 

$$\text{out} = \overline{A \cdot B}$$

 

Not gate we built in the last slide

 

Formal proof in Textbook Appendix A1.3


How to construct And, Or and Not from Nand



From this



| A | B | out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

 

$$out = \overline{A \cdot B}$$


Formal proof in Textbook Appendix A1.3

How to construct And, Or and Not from Nand




From this

| A | B | \bar{A} | \bar{B} | out |
|---|---|-----------|-----------|-----|
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |

 


$$out = \overline{A \cdot B}$$

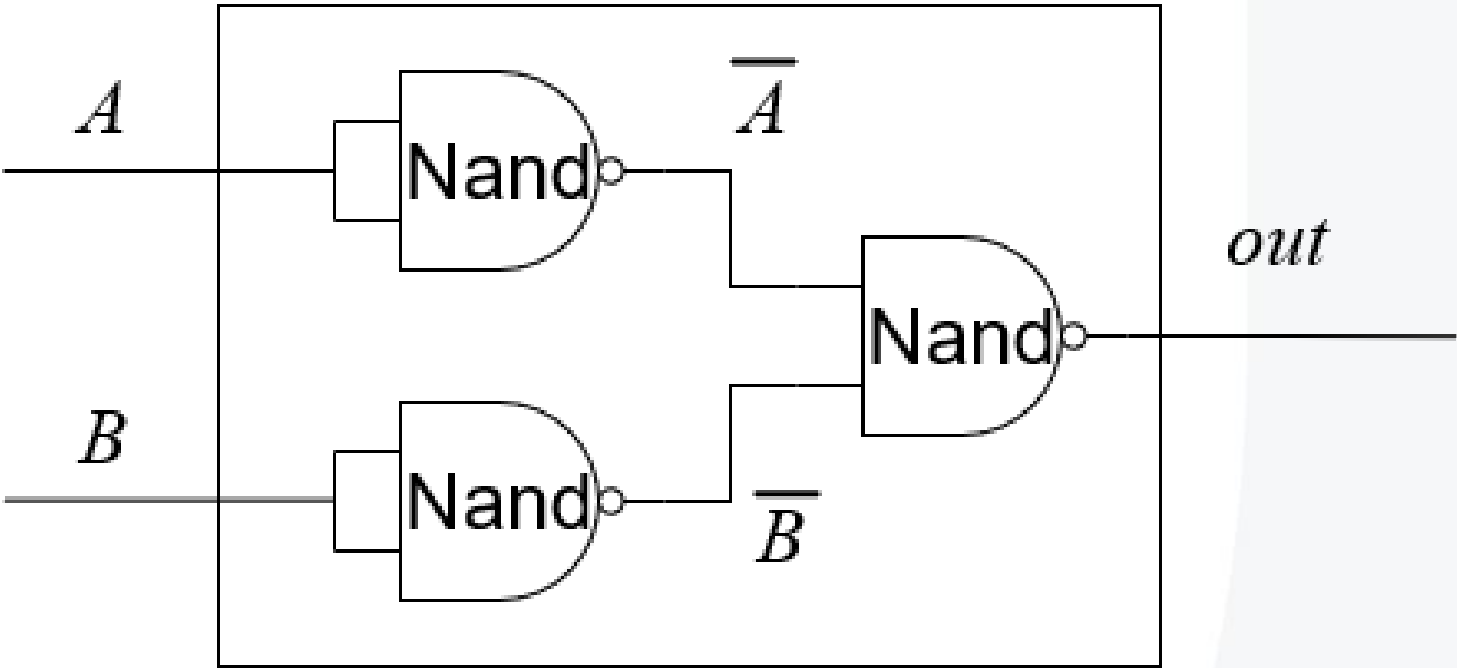

Add one Not gate
to each of the A
and B

 
$x+y = \overline{\overline{x} \cdot \overline{y}}$
De Morgan's Theorem




Formal proof in Textbook Appendix A1.3

Boolean Functions: Summary

 - Each Boolean function has a canonical representation
- The canonical representation is expressed in terms of And, Or, Not
- And, Not, Or can be expressed in terms of Nand alone (or Nor)
- Every Boolean function can be realised by a standard circuit consisting of Nand gates only
- Mass production
- Universal building blocks, unique topology



 
Exercise: Canonical Form Boolean Expression for 1-bit Full Adder




| x | y | Cin | Sum | Cout |
|---|---|-----|-----|------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |



Exercise: Build Nand using And, Or, Not

 

Exercise: Build Nor using And, Or, Not

 

This Week

- Review Chapter 1 of the Textbook
- Start Assignment 1 (available from Wednesday week 1)
- Workshops start in week 2
- Week 2 quiz due before Thursday lecture.

